

EXP NO: 06

VERIFICATION OF MAXIMUM POWER TRANSFER

DATE:

26/9/2025

THEOREMAIM:

To measure the power absorbed in load and to verify that the power absorbed in a load is maximum only when load resistance is equal to the source resistance.


APPARATUS REQUIRED:

S.NO	Name of the Apparatus	Range / Rating	Quantity
1	voltmeter	(0-15V) MC	1
2	Ammeter	(0-500mA) MC	1
3	Resistors	560 $\Omega$ ,	2
		470 $\Omega$	1
4	RPS (DC supply)	0-15V	1


PROCEDURE:

1. Make connection as per the circuit diagram.
2. change the resistors  $R_L$  whose value close to  $R_{th}$ , measure the corresponding  $V_L$ ,  $I_L$  and calculate  $P_L$  and enter into the table (2).
3. Plot a graph between  $R_L$  and  $P_L$  and find the  $R_L$  corresponding to maximum power transfer
4. verify the measured values of  $R_L$  at maximum power transfer as same as calculated and found graphically.
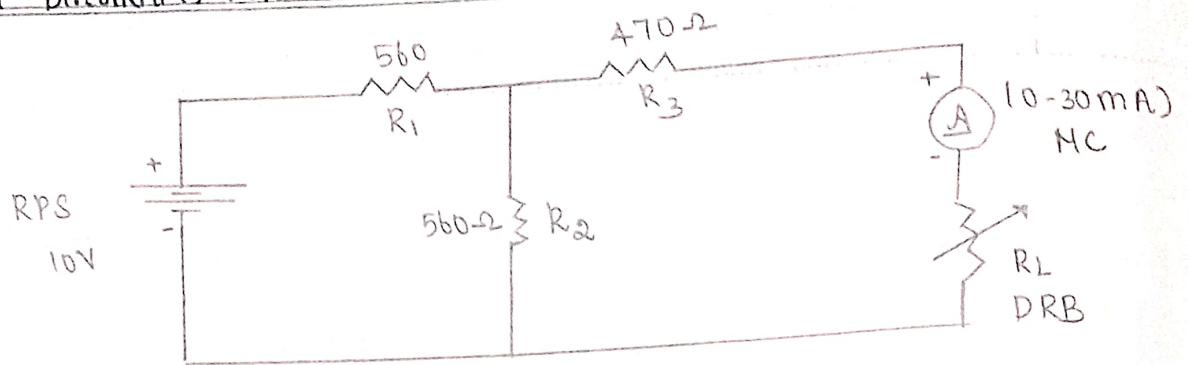
## CIRCUIT DIAGRAM: FOR MAXIMUM POWER TRANSFER THEOREM



## MODEL GRAPH:

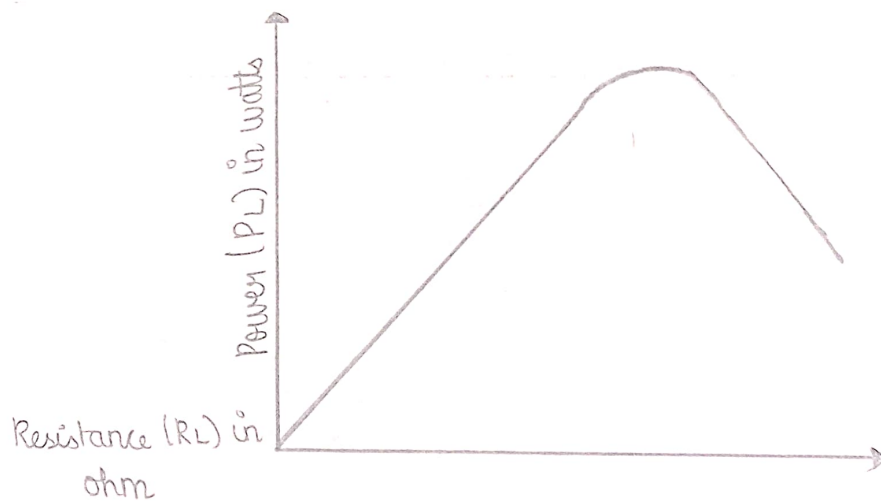



TABLE(2): FOR PRACTICAL (CALCULATION):

S-NO	Load resistance ( $R_L$ ) in $\Omega$	Load current ( $I_L$ ) in amps	Load voltage ( $V_L$ ) in volts	Load power ( $P_L$ ) in Watts
1	1k $\Omega$	2.96mA	2.96V	8.76mW
2	150k $\Omega$	5.53mA	0.995V	6.60mW
3	100k $\Omega$	6.00mA	0.6V	3.6mW
4	470k $\Omega$	4.13mA	1.94V	8.01mW
5	5k $\Omega$	0.85mA	4.335V	3.68mW

CALCULATION:-

$$V_{Th} = \frac{V \times R_2}{R_1 + R_2} = \frac{10 \times 560}{560 + 560} = \underline{5V}$$

$$R_{Th} = \frac{560 \times 560}{2(560)} + 470 = 280 + 470 = \underline{750\Omega}$$

$$R_L = R_{Th}$$

$$P_L = \frac{(V_{Th})^2}{4(R_{Th})} = \frac{(5)^2}{4 \times 750} = \frac{25}{4 \times 750} = \frac{25}{3000}$$

$$= \underline{8.33mW}$$

$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{5}{1500} = 0.0033A //$$

$$I_L = 3.33mA$$

$$V_L = I_L \times R_L = 3.33 \times 10^{-3} \times 750$$

$$V_L = 2.5V$$



RESULT:

The maximum power transfer theorem is verified practically and theoretically.